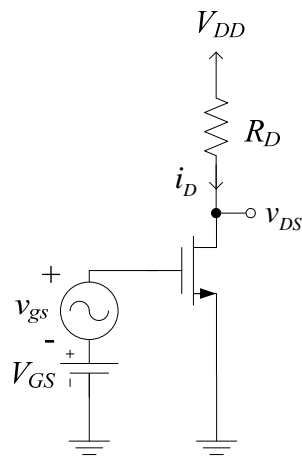


Lecture 28: MOSFET as an Amplifier. Small-Signal Equivalent Circuit Models.

As with the BJT, we can use MOSFETs as **AC small-signal amplifiers**. An example is the so-called conceptual MOSFET amplifier shown in Fig. 4.34:



(Fig. 4.34)

This is only a “conceptual” amplifier for **two** primary reasons:

1. The bias with V_{GS} is impractical. (Will consider others later.)
2. In ICs, resistors take up too much room. (Would use another triode-region biased MOSFET in lieu of R_D .)

To operate as a small-signal amplifier, we bias the MOSFET in the saturation region. For the analysis of the DC operating point, we set $v_{gs} = 0$ so that from (4.22) with $\lambda = 0$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 \quad (4.20), (1)$$

From the circuit $V_{DS} = V_{DD} - I_D R_D \quad (4.55), (2)$

For operation in the saturation region

$$v_{GD} \leq V_t \Rightarrow v_{GS} - v_{DS} \leq V_t$$

or

$$v_{DS} \geq v_{GS} - V_t \quad (4.18),(3)$$

where the total drain-to-source voltage is

$$v_{DS} = \underbrace{V_{DS}}_{\text{bias}} + \underbrace{v_{ds}}_{\text{AC}}$$

Similar to what we saw with BJT amplifiers, we need make sure that (3) is satisfied for the **entire signal swing** of v_{ds} .

With an AC signal applied at the gate

$$v_{GS} = V_{GS} + v_{gs} \quad (4.56),(4)$$

Substituting (4) into (4.20)

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 = \frac{1}{2} k_n' \frac{W}{L} [(V_{GS} - V_t) + v_{gs}]^2 \quad (5)$$

$$\begin{aligned} &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 + \frac{2}{2} k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \quad (4.57),(6) \\ &\quad = I_D \text{ (DC)} \quad \quad \quad \text{(time varying)} \end{aligned}$$

The last term in (6) is **nonlinear** in v_{gs} , which is undesirable for a linear amplifier. Consequently, for linear operation we will require that the last term be “small”:

$$\frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \ll k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}$$

or

$$\underline{v_{gs} \ll 2(V_{GS} - V_t)} \quad (4.58),(7)$$

If this small-signal condition (7) is satisfied, then from (4.57) the total drain current is approximately the **linear summation**

$$i_D \approx \underbrace{I_D}_{\text{DC}} + \underbrace{i_d}_{\text{AC}} \quad (4.60), (8)$$

where

$$i_d = k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}. \quad (9)$$

From this expression (9) we see that the AC drain current i_d is related to v_{gs} by the so-called **transistor transconductance, g_m** :

$$g_m \equiv \frac{i_d}{v_{gs}} = k_n' \frac{W}{L} (V_{GS} - V_t) \text{ [S]} \quad (4.61), (10)$$


which is sometimes expressed in terms of the **overdrive voltage** $V_{OV} \equiv V_{GS} - V_t$

$$g_m = k_n' \frac{W}{L} V_{OV} \text{ [S]} \quad (4.62), (11)$$

Because of the V_{GS} term in (10) and (11), this g_m **depends on the bias**, which is just like a BJT.

Physically, this transconductance g_m equals the **slope** of the i_D - v_{GS} characteristic curve at the Q point:

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} \quad (4.63), (12)$$

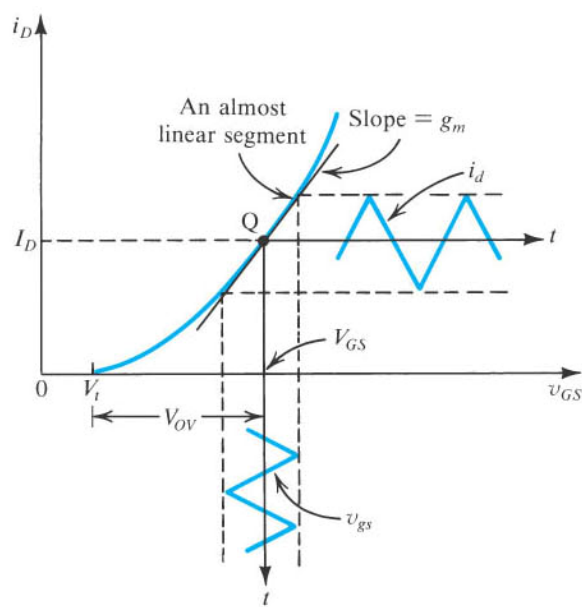

(Fig. 4.35)

Lastly, it can be easily show that for this conceptual amplifier in Fig. 4.34,


$$\frac{v_d}{v_{gs}} = -g_m R_D \quad (4.65), (13)$$

Consequently, $A_v \propto g_m$, which is the same result we found for a similar BJT conceptual amplifier [see (5.103)].

MOSFET Small-Signal Equivalent Models

For circuit analysis, it is convenient to use equivalent small-signal models for MOSFETs – as it was with BJTs.

In the saturation mode, the MOSFET acts as a **voltage controlled current source**. The control voltage is v_{gs} and the output current is i_D , which gives rise to this small-signal **π model**:

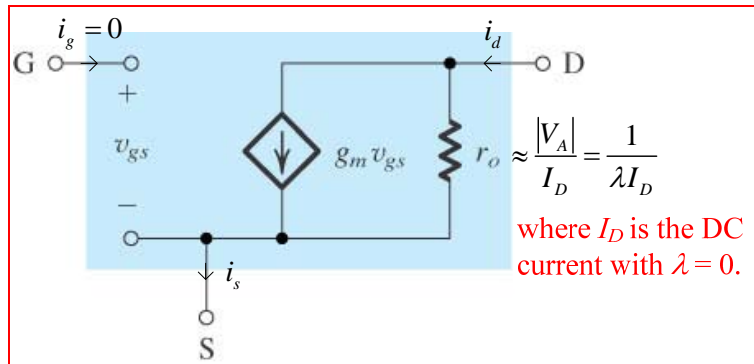

(Fig. 4.37b)

Things to note from this small-signal model include:

1. $i_g = 0$ and $v_{gs} \neq 0 \Rightarrow$ infinite input impedance.
2. r_o models the finite output resistance. Practically speaking, it will range from $\approx 10 \text{ k}\Omega \rightarrow 1 \text{ M}\Omega$. Note that it depends on the bias current I_D .
3. From (10) we found

$$g_m = k_n' \frac{W}{L} (V_{GS} - V_t) \quad (14)$$


Alternatively, it can be shown that

$$g_m = \frac{I_D}{V_{eff}} = \frac{I_D}{(V_{GS} - V_t)/2} \quad (4.71), (15)$$

which is similar to $g_m = I_C / V_T$ for BJTs.

One big difference from BJTs is $V_T \approx 25 \text{ mV}$ while $V_{eff} = 0.1 \text{ V}$ or greater. Hence, for the same bias current **g_m is much larger for BJTs** than for MOSFETs.

A small-signal **T model** for the MOSFET is shown in Fig. 4.40:

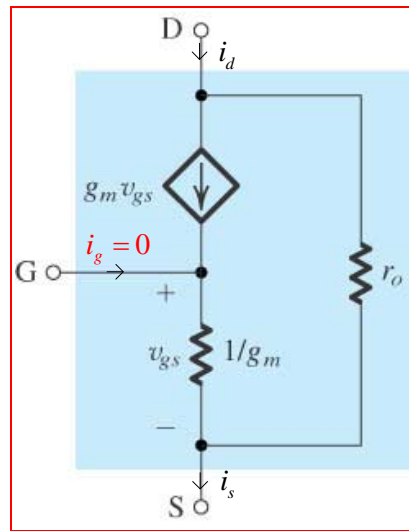

(Fig. 4.40a)

Notice the direct connection between the gate and both the dependent current source and $1/g_m$. While this model is correct, we've **added the explicit boundary condition that $i_g = 0$** to this small-signal model.


It isn't necessary to do this because the currents in the two vertical branches are both equal to $g_m v_{gs}$, which means $i_g = 0$. But adding this condition $i_g = 0$ to the small-signal model in Fig. 4.40a makes this explicit in the circuit calculations. (The T model usually shows this direct connection while the π model usually doesn't.)

MOSFETs have **many advantages** over BJTs including:

1. High input resistance
2. Small physical size
3. Low power dissipation

4. Relative ease of fabrication.

One can **combine** advantages of both technologies (BJT and MOSFET) into what are called BiCMOS amplifiers:

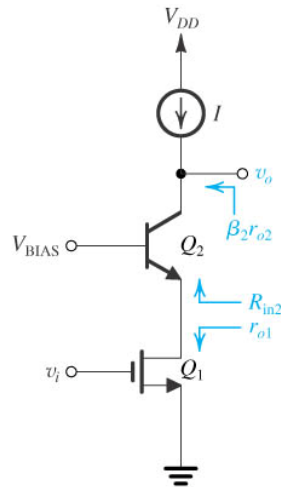

(Fig. 6.46a)

Such a combination provides a very large input resistance from the MOSFET and a large output impedance from the BJT.