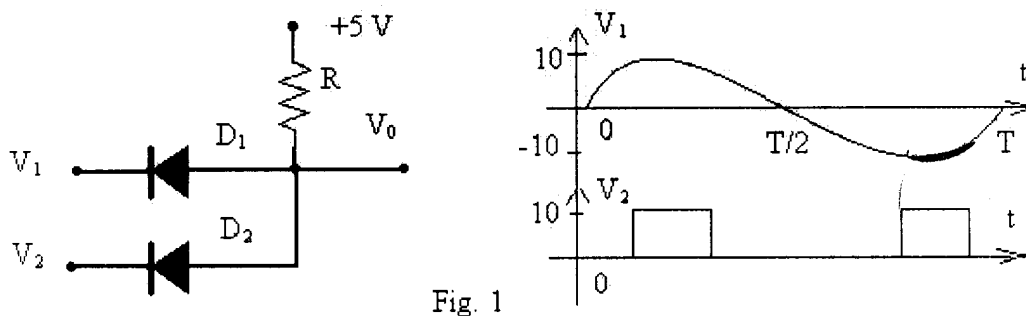



Student Name \_\_\_\_\_

Faculty No: \_\_\_\_\_


1. Signals applied to the circuit of Fig. 1 are shown. Define and plot the output signal  $V_o$ , assuming ideal diodes.



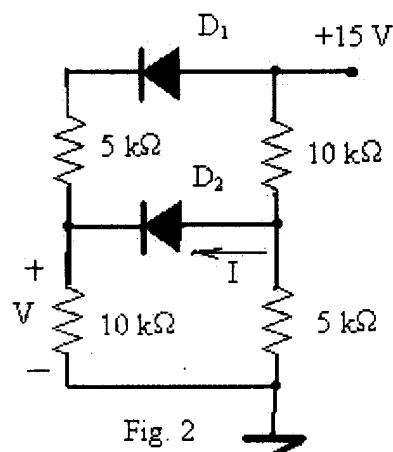2. Find the values of  $I$  and  $V$  for the circuit of Fig.2 assuming that the diodes are ideal.



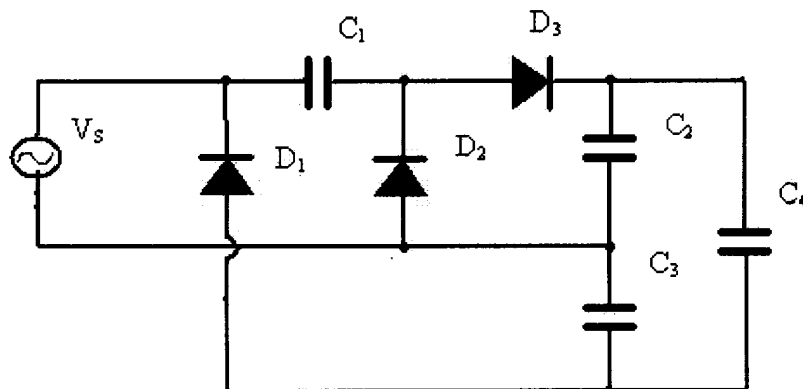3. The circuit shown in Fig.3 has a **20 V** peak sinusoidal input signal. Determine  $V_{C1}$ ,  $V_{C2}$ ,  $V_{C3}$  and  $V_{C4}$  for the circuit. Assume that the diodes are ideal.



4. Determine the range of  $V_i$  that will maintain the Zener diode of Fig. 4 in the "ON" state. ( $V_Z = 10\text{ V}$ ,  $I_{ZM} = 20\text{ mA}$ ).


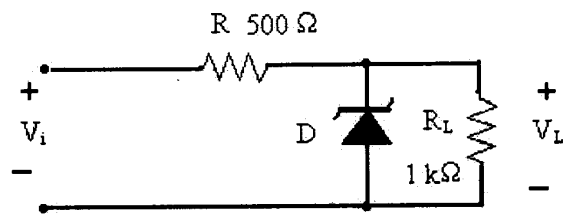



Fig.4

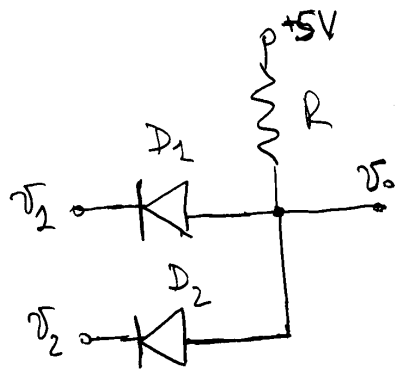5. Calculate the voltage gain ( $A_v = V_o/V_i$ ) for the common base network, if ac input resistance  $R_i = 50\ \Omega$ , ac output resistance  $R_o = 500\text{ k}\Omega$  and load resistance  $R_L = 2\text{ k}\Omega$ . Assume, that  $\alpha = 1$ .


20 points (each 4 points).  
**Good Luck!**



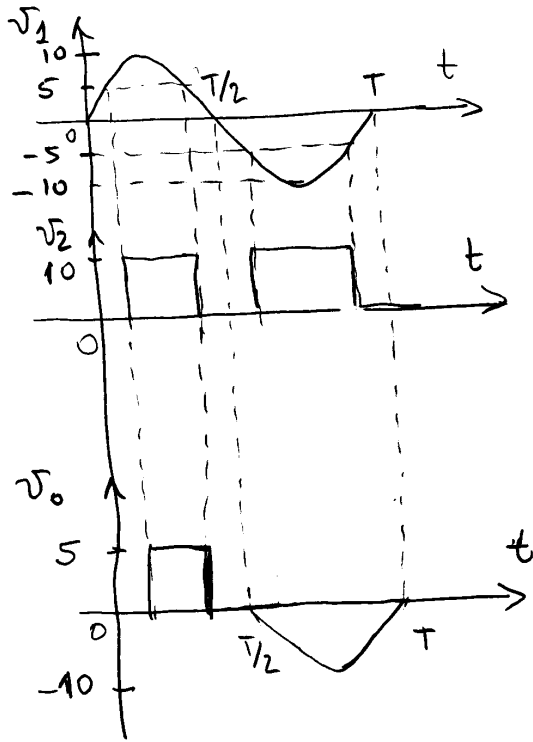1 Signals applied to the circuit of Fig. 1 are shown. Define and plot the output signal, assuming ideal diodes.



Solution:

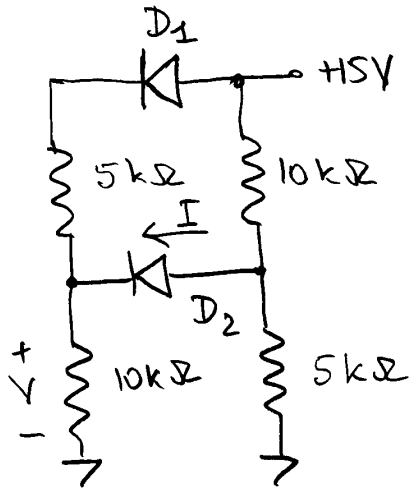


2. Find the values of  $I$  and  $V$  for the circuit of Fig. 2 assuming that the diodes are ideal.

### Solution

Voltage source of +15V opens  $D_1$  and due to the current in voltage divider stabilize  $V = +10V$ .

From the other side there is voltage 5V across resistor of  $5k\Omega$ . The  $D_2$  is in "OFF" state, then

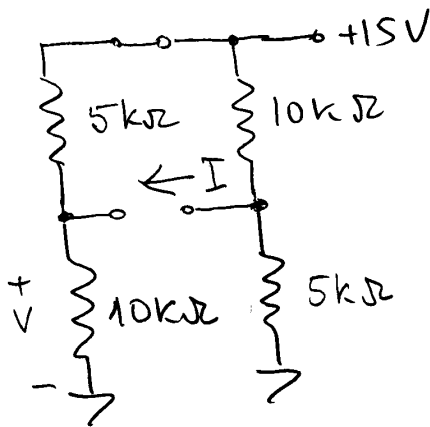
equivalent circuit is of form shown, and current  $I = 0mA$



### Answers:

$$V = 10V$$

$$I = 0A$$

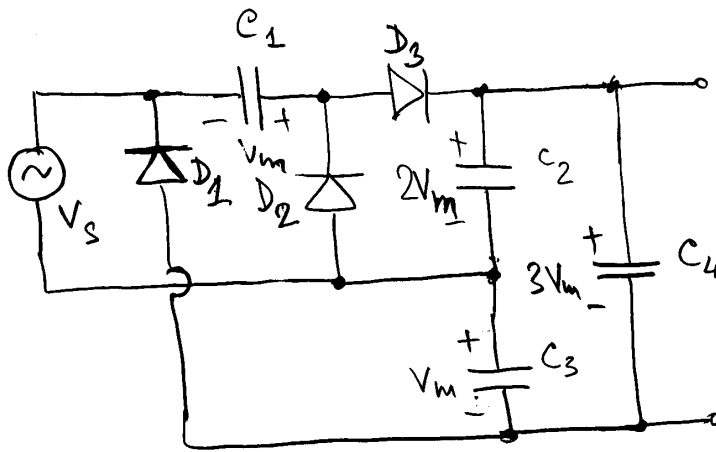


3. The circuit shown in Fig. 3 has a 20 V peak input signal. Determine  $V_{C1}$ ,  $V_{C2}$ ,  $V_{C3}$  and  $V_{C4}$

for the circuit. Assume that the diodes are ideal.
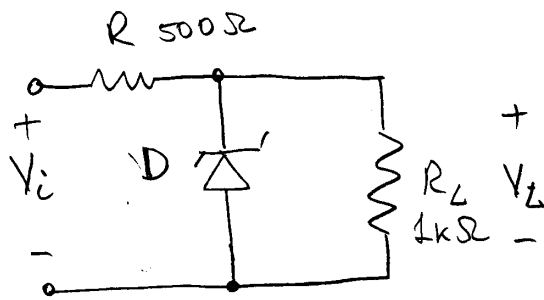
### Solution

- When acts negative half-wave of the input signal, capacitors  $C_1$  and  $C_3$  charges up to  $V_m = 20\text{ V}$  through  $D_2$  and  $D_1$  respectively with polarity shown.
- When acts positive half-wave of the input signal,  $C_2$  charges through  $D_3$  up to  $2V_m = 40\text{ V}$ .
- Because  $C_2$  and  $C_3$  are in series and this branch is in parallel to  $C_4$ , total output voltage is  $V_m + 2V_m = 3V_m = 3 \cdot 20 = 60\text{ V}$



4. Determine the range of  $V_i$  that will maintain the Zener diode of Fig. 4. in the "ON" state.  
 ( $V_Z = 10\text{ V}$ ,  $I_{Zm} = 20\text{ mA}$ )

Solution

$$V_{i\min} = \frac{R_L + R}{R_L} V_Z = \frac{(1 + 0.5) \cdot 10^3}{1 \cdot 10^3} \cdot 10 = 15\text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{10}{1 \cdot 10^3} = 10\text{ mA}$$

$$I_{R\max} = I_{Zm} + I_L = 20 + 10 = 30\text{ mA}$$

$$\begin{aligned} V_{i\max} &= I_{R\max} \cdot R + V_Z = 30 \cdot 0.5 \cdot 10^{-3} \cdot 10^3 + 10 = \\ &= 15 + 10 = 25\text{ V} \end{aligned}$$

5. Calculate the voltage gain ( $A_v = V_o/V_i$ ) for the common base network, if  $R_i = 50\Omega$ ,  $R_o = 500k\Omega$  and  $R_L = 2k\Omega$ . Assume that  $\alpha = 1$ .

### Solution

1. Input current is

$$I_i = \frac{V_i}{R_i} = \frac{V_i}{50} \text{ A}$$

2. Assuming  $\alpha = 1$ , then  $I_{out} = I_{input}$  and

$$\begin{aligned} V_o &= I_o \cdot R_L = I_i R_o = \frac{V_i}{50} 2 \cdot 10^3 \\ &= 40 V_i \text{ V} \end{aligned}$$

3. Voltage gain is

$$A_v = \frac{V_o}{V_i} = \frac{40 V_i}{V_i} = 40$$