

Part II

Devices – Diode, BJT, MOSFETs

4

Semiconductor

- Semiconductor
 - The number of charge carriers available to conduct current¹ is between that of conductors and that of insulators.
 - Semiconductor is basically a pn junction where the p -type silicon contacts with the n -type silicon.
 - * Different types of silicon are created by implanting different dopings.

4.1 Intrinsic Silicon

- Figure 4.1 shows the 2-D structure of the intrinsic silicon.
 - Each atom shares each of its 4 valence electrons with a neighboring atom.
 - Atoms are held in their positions by covalent bounds.
 - * Covalent bounds are intact at sufficient low temperature.
 - No free electrons are available to conduct current.
 - * Covalent bounds may be broken by thermal ionization.
- Thermal ionization at room temperature (Figure 4.2)
 - An electron leaves its parent atom; thus, a positive charge is left with the atom.
 - * The ionization results in free electrons and holes in equal numbers.
 - * At room temperature, the silicon has 1.5×10^{10} carries/cm³ and about 5×10^{22} atoms/cm³.
 - The concentration of free electrons n is equal to the concentration of free holes p .

$$n = p = n_i \quad (4.1)$$

- n_i is the number of free electrons (or holes) per cm³ in intrinsic silicon at a given temperature.

$$n_i^2 = BT^3 e^{-E_G/kT} \quad (4.2)$$

¹The current of 1 ampere is defined as 1 coulomb of electric charge (which consists of about 6.242×10^{18} electrons) drifts every second at the same velocity through the imaginary plane through which the conductor passes.

 


Figure 4.1: Two-dimensional representation of the silicon crystal.

 


Figure 4.2: Electrons and holes generated by thermal ionization.

- B is a material dependent parameter = 5.4×10^{31} for silicon.
- E_G is the bandgap energy = 1.12 electron volts (eV), representing the minimum energy required to break a covalent bond and generate an electron-hole pair.
- k is Boltzmann's constant = 1.38×10^{-23} joules/kelvin.
- T is absolute temperature in Kelvins = $273 + \text{temperature in } ^\circ\text{C}$.
- An electron from a neighboring atom may be attracted and create a new hole.
 - * Ionization rate is equal to recombination rate in thermal equilibrium.
- The process repeats with a hole moves through the silicon and conducts current.

- * Holes and electrons move through silicon by diffusion and drift mechanisms.

 


Figure 4.3: Illustration of diffusion mechanism: (a) a bar of intrinsic silicon, and (b) the hole concentration profile.

- Diffusion mechanism

- Random motion due to thermal agitation.
- Non-uniform concentrations of free electrons and holes cause a net flow of charge (or diffusion current).
- The current density of the hole diffusion current at any point.

$$J_p = -qD_p \frac{dp}{dx} \quad (4.3)$$

- * J_p in A/cm² is the current density, i.e., the current per unit area of the plane perpendicular to the x -axis.²
- * p is the concentration of free holes.
- * q is the magnitude of electron charge = $1.6 \times 10^{-19}C$.
- * D_p is the diffusion constant of holes = $12\text{cm}^2/\text{s}$.
- * A negative (dp/dx) results in a positive current in the x direction.
- The magnitude of the electron diffusion current at any point.³

$$J_n = qD_n \frac{dn}{dx} \quad (4.4)$$

- * J_n in A/cm² is the current density, i.e., the current per unit area of the plane perpendicular to the x -axis.
- * n is the concentration of free electrons.
- * q is the magnitude of electron charge = $1.6 \times 10^{-19}C$.
- * D_n is the diffusion constant of electrons = $34\text{cm}^2/\text{s}$.

²The unit of J_p can be derived from the formulation $J_p = -q(\text{charge})D_p(\text{cm}^2/\text{s})dp(\text{difference of the number of the holes}/\text{cm}^3)/dx(\text{cm}) = (\text{charges/s})/\text{cm}^2 = \text{A}/\text{cm}^2$.

³To double check.

* A negative (dn/dx) results in a negative current in the x direction.

- Drift mechanism

- Carrier drift occurs when an electric field is applied across a piece of silicon.
- Free electrons and holes are accelerated by electric field and acquire a drift velocity (superimposed on the velocity of thermal motion).

$$v_{drift} = u_p E \quad (4.5)$$

* u_p is the mobility of holes in $\text{cm}^2/\text{V}\cdot\text{s} = 480$.

* E is the strength of electric field in V/cm .

- The current density of holes in A/cm^2 .

$$J_{p-drift} = qp u_p E \quad (4.6)$$

- The current density of electrons in A/cm^2 .

$$J_{n-drift} = qn u_n E \quad (4.7)$$

* u_n is the mobility of electrons in $\text{cm}^2/\text{V}\cdot\text{s} = 1350$.

- The total drift current density in A/cm^2 .

$$J_{drift} = q(pu_p + nu_n)E \quad (4.8)$$

* A form of Ohm's law with the resistivity $\rho = 1/q(pu_p + nu_n)$ in $\Omega \cdot \text{cm}$.

- Einstein relationship

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T \quad (4.9)$$

4.2 Doped Silicon

- Doped silicon

- Achieved by introducing a small number of impurity atoms.

- In n -type silicon, the majority of carriers are the negatively charged electrons.

- Achieved by implanting pentavalent impurity (also known as donor).
- In thermal equilibrium

* The concentration of free electrons $n_{n0} \simeq N_D$.

* The product of electron and hole concentrations remains constant.

• p_{n0} is a function of temperature.

$$n_{n0}p_{n0} = n_i^2 \quad (4.10)$$

 


Figure 4.4: Doped *n*-type and *p*-type semiconductor.

- In *p*-type silicon, the majority of carriers are the positively charged holes.
 - Achieved by implanting trivalent impurity (also known as acceptor).
 - In thermal equilibrium
 - * The concentration of free holes $p_{p0} \simeq N_A$.
 - * The product of electron and hole concentrations remains constant.
 - n_{p0} is a function of temperature.

$$n_{p0}p_{p0} = n_i^2 \quad (4.11)$$

- A piece of *p*-/*n*-type silicon is electrically neutral.
 - The majority of free carriers are neutralized by bound charges associated with impurity atoms.

5

Diode

A two-terminal device with a nonlinear $i - v$ characteristic.

- Main applications
 - Rectifier.
 - Generation of DC voltages from AC power.
 - Generation of signals of various waveforms.
- Circuit symbol

 


Figure 5.1: The symbol of diode.

5.1 Physical Structure

- Diode is basically a pn junction device.

5.1.1 The pn Junction Under Open Circuit

- Figure 5.2 shows the pn junction with open circuit.
- Diffusion current I_D .
 - Generated by the movement of majority carriers.
 - Electrons diffuse across the junction from the n side to the p side.
 - Holes diffuse across the junction from the p side to the n side.
 - The two currents add together to form a diffusion current I_D with direction from p side to n side.
- Depletion region.
 - Electrons diffuse across the junction and combine with majority holes.

 


Figure 5.2: (a) The pn junction with no applied voltage (open-circuited terminals). (b) The potential distribution along an axis perpendicular to the junction.

- * In p -type silicon, there will be a region depleted of holes and containing uncovered bound negative charge.
- Holes diffuse across the junction and combine with majority electrons.
- * In n -type silicon, there will be a region depleted of electrons and containing uncovered bound positive charge.
- The bound charges on both sides of the depletion region forms a junction built-in voltage.

$$V_0 = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right) \quad (5.1)$$

- * N_A and N_D are the doping concentrations of the p side and the n side, respectively.
- * The built-in voltage V_0 for silicon at room temperature is $0.6 \sim 0.8V$.
- * The electric field acts as a barrier that must be overcome for holes and electrons to diffuse.
- Depletion regions exist in both sides with equal amount of charges.
- * The depletion layer will extend deeper into the more lightly doped material.

$$\begin{aligned} qx_p A N_A &= qx_n A N_D \\ \frac{x_n}{x_p} &= \frac{N_A}{N_D} \end{aligned} \quad (5.2)$$

 


Figure 5.3: The pn junction excited by a constant-current source I in the reverse direction. To avoid breakdown, I is kept smaller than I_S . Note that the depletion layer widens and the barrier voltage increases by V_R volts, which appears between the terminals as a reverse voltage.

- * The width of the depletion region of an open-circuit junction is typically in the range of $0.1\mu\text{m}$ to $1\mu\text{m}$.

$$W_{dep} = x_n + x_p = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) V_0} \quad (5.3)$$

- Drift current $I_{S_{drift}}$.
 - Achieved by the movement of thermally generated minority carriers.
 - Electrons in p -silicon diffuse to the depletion region and got swept to the n -silicon.
 - Holes in n -silicon diffuse to the depletion region and got swept to the p -silicon.
 - The two currents add together to form a drift current $I_{S_{drift}}$ with direction from n side to p side.
 - $I_{S_{drift}}$ depends on temperature instead of the built-in voltage V_0 .
- In thermal equilibrium and under open circuit condition, $I_{S_{drift}} = I_D$.
 - If $I_D > I_{S_{drift}}$, the uncovered bound charges will increase and the voltage across the depletion region will increase. This in turn causes I_D to decrease.
 - If $I_{S_{drift}} > I_D$, the uncovered bound charges will decrease and the voltage across it will decrease. This in turn causes $I_{S_{drift}}$ to decrease.

5.1.2 The pn Junction Under Reverse-Bias

- Figure 5.3 depicts the pn junction with reverse bias.
- Electrons flows from the n -side to the p -side through the external circuit.
 - Electrons leaving the n -side cause an increase in the positive bound charges.
 - Holes leaving the p -side cause an increase in the negative bound charges.

- A increase in the width of, and the charges stored in, the depletion region.
 - * A higher barrier voltage results in the decrease of I_D .
- In thermal equilibrium, $I_{S_{drift}} - I_D = I$.
- Depletion capacitance
 - As the voltage across the pn junction changes, the charges stored in the depletion layer changes.¹
 - The charges q_J stored in the depletion layer.
 - * A function of V_R .
 - * A is the cross-sectional area of the junction.

$$\begin{aligned}
 q_J &= q_N \\
 &= qN_D x_n A \\
 &= q \frac{N_D N_A}{N_D + N_A} W_{dep} A \\
 &= q \frac{N_D N_A}{N_D + N_A} A \sqrt{\frac{2\epsilon_s}{q} \left(\frac{N_A + N_D}{N_A N_D} \right) (V_0 + V_R)}
 \end{aligned} \tag{5.4}$$

- The depletion capacitance.

$$C_j = \frac{dq_J}{dV_R} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}} \tag{5.5}$$

- * The capacitance varies with the bias point.
- * C_{j0} is the value of C_j with no voltage applied.

 


Figure 5.4: The charge stored on either side of the depletion layer as a function of the reverse voltage V_R .

¹Capacitance $C = \Delta Q / \Delta V$.

5.1.3 The pn Junction in the Breakdown Region

- A sufficiently high junction voltage develops and many carriers are created by zener or avalanche mechanism so as to support any value of reverse current.
 - It is not a destructive process as long as the maximum power dissipation is not exceeded.
- Zener effect
 - It occurs when the breakdown voltage $V_Z < 5V$.
 - Electric field in the depletion regions increases to a point where it can break covalent bounds and generate electron-hole pairs.
 - * The holes will be swept into the n side.
 - * The electrons will be swept into the p side.
 - * These electrons and holes constitute a reverse current across the junction.
- Avalanche effect
 - It occurs when the breakdown voltage $V_Z > 7V$.
 - Minority carriers gain sufficient energy by the electric field to break the covalent bounds.
 - * The carriers may have sufficient energy to cause other carriers to be liberated in another ionizing collision.

5.1.4 The pn Junction Under Forward Bias Conditions

 


Figure 5.5: The pn junction excited by a constant-current source supplying a current I in the forward direction. The depletion layer narrows and the barrier voltage decreases by V volts, which appears as an external voltage in the forward direction.

- Figure 5.5 depicts the pn junction with forward bias.
- The barrier voltage is reduced since majority carriers neutralize some of the uncovered bound charge.
 - Majority carriers are supplied to both sides through the external circuit.
 - Holes are injected into the n -side and electrons are injected into the p -side.

- * The concentration of minority carriers at both sides will exceed the thermal equilibrium, p_{n0} and n_{p0} .
 - * The excess concentration decreases exponentially as one moves away from the junction.
 - * In the steady state, the concentration profile of excess minority carriers remains constant.
- Diffusion current I_D increases until the equilibrium is achieved with $I_D - I_{S_{drift}} = I$.

 


Figure 5.6: Minority-carrier distribution in a forward-biased pn junction. It is assumed that the p region is more heavily doped than the n region.

- Diffusion capacitance
 - In steady state, a certain amount of excess minority-carrier charge is stored in each of the p and n bulk region. If the terminal voltage changes, this charge will have to change before a steady state is achieved.
- $$C_d = \frac{\tau_T}{V_T} I \quad (5.6)$$
- * τ_T is the mean transit time of the diode, which is related to the excess minority carrier life time τ_p and τ_n .
 - * I is the diode current.
 - The diffusion capacitance is negligibly small when the diode is reverse bias.
 - Depletion capacitance
 - As the voltage across the pn junction changes, the charge stored in the depletion layer changes.

$$C_j = 2C_{j0} \quad (5.7)$$

5.2 Characteristics

 


Figure 5.7: The diode $i - v$ relationship with some scales expanded and others compressed.

5.2.1 Forward Bias

- Forward region of operation is entered when the terminal voltage v is positive.
- The $i - v$ curve in forward region is closely approximated by

$$i = I_S(e^{v/nV_T} - 1) \quad (5.8)$$

– I_S is called saturation current (or scale current).

$$I_S = Aqn_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right) \quad (5.9)$$

- * A function of temperature.
 - n_i is the concentration of electrons in intrinsic silicon, which depends on the temperature as suggested by Eq. (4.2).
 - Generally, I_S doubles in value for every 5°C rise in temperature.
- * A factor proportional to the cross-sectional area of the diode.
 - A is the cross-sectional area of the pn junction.

- V_T is called thermal voltage, which is $\simeq 25\text{mV}$ in room temperature (20°C).

$$V_T = \frac{kT}{q} \quad (5.10)$$

- * k = Boltzmann's constant = 1.38×10^{-23} joules/kelvin.
- * T = Absolute temperature in Kelvins = $273 + \text{temperature in } ^\circ\text{C}$.
- * q = Magnitude of electronic charge = 1.60×10^{-19} in coulomb.
- n is a value between 1 and 2
 - * A value depends on the material and physical structure of the diode.
 - * By default, $n = 1$ unless otherwise specified.
- If $i \gg I_S$, the $i - v$ curve in forward regions can be further approximated by the exponential relationship.

$$i \simeq I_S e^{v/nV_T} \quad (5.11)$$

- The logarithmic form of $i - v$ characteristic.
 - * The $v - i$ curve is a straight line on semilog paper² with a slope of $2.3nV_T$.

$$v \simeq nV_T \ln\left(\frac{i}{I_S}\right) = 2.3nV_T \log_{10}\left(\frac{i}{I_S}\right) \quad (5.12)$$

- A factor of 10 increases in current leads to the increase of voltage drop by a factor of $2.3nV_T$, which is $\simeq 60\text{mV}$ in room temperature and with $n = 1$.

$$\begin{aligned} V_2 - V_1 &\simeq nV_T \ln\left(\frac{I_2}{I_1}\right) \\ \frac{I_2}{I_1} &\simeq e^{(V_2 - V_1)/nV_T} \end{aligned} \quad (5.13)$$

- Cut-in Voltage
 - A consequence of the exponential $i - v$ relationship.
 - * When $v \ll nV_T$, the current i is negligible.
 - * When $v \gg nV_T$, the current i grows exponentially. (Fully Conducting)
 - * Example: Cut-in voltage $V_{\text{cut-in}}$ in Figure 5.7 is $0.5V$.
 - Cut-in voltage varies with temperature for a given diode.
- Fully Conducting
 - The voltage v is greater than $V_{\text{cut-in}}$ and the current i grows exponentially.
 - Voltage drop varies with temperature for a given diode.

5.2.2 Reverse Bias

- Reverse-bias is entered when the terminal voltage v is made negative.

²The vertical axis is a linear axis for v and the horizontal axis is a log axis for i .

 


Figure 5.8: The temperature dependency of the diode forward characteristic.

- The reverse current i approximates $-I_s$.
 - The term e^{v/nV_T} in Eq. (5.8) becomes negligible as $v \rightarrow -\infty$.
 - A function of temperature.
 - * The reverse current doubles in value for every 10°C rise in temperature.
 - A large part of reverse current is due to leakage effects.
 - * Leakage currents are proportional to the junction area.
 - * Real diodes exhibit reverse currents that are much larger than I_s .

5.2.3 Breakdown Region

- Breakdown region is entered when the reverse voltage exceeds breakdown voltage V_{ZK} .
- The reverse current i increases rapidly with very small increase in voltage drop.
 - A good property for voltage regulation.

5.3 Model

5.3.1 Large Signal Model

Ideal Diode

- Forward biased
 - Short circuit with zero voltage drop when $v > 0$.
- Reverse biased
 - Open circuit with zero current when $v < 0$.

Exponential Model

- The most accurate description of the diode operation in forward region.

Table 5.1: Comparison of the models in the diode forward region.

Model	$i - v$ Graph	Equivalent Circuit
Ideal		
Exponential		
Piecewise-linear	<p style="text-align: center;">(a)</p>	<p style="text-align: center;">(b)</p>
Constant Voltage Drop	<p style="text-align: center;">(a)</p>	<p style="text-align: center;">(b)</p>
Small Signal		

 


Figure 5.9: The i-v characteristic of the ideal diode.

 


Figure 5.10: The characteristic of the ideal diode with positive and negative voltages applied.

- The most difficult one to use due to nonlinear nature.
- Pencil-and-paper solutions: (1) graphical analysis, and (2) iterative analysis.

Example 5.1 *Given the circuit to be analyzed as in Figure 5.11, find out the I_D and V_D using graphical analysis.*

 


Figure 5.11: A simple circuit used to illustrate graphical analysis with exponential model.

1. Assume V_{DD} is greater than $0.5V$ so that the diode operates in forward bias region.

$$I_D = I_S e^{V_D/nV_T} \quad (5.14)$$

2. Further, writing a Kirchhoff loop equation, we can obtain the other equation that governs the circuit operation.

$$I_D = \frac{V_{DD} - V_D}{R} \quad (5.15)$$

3. Graphical analysis is performed by plotting Eq. (5.14) and Eq. (5.15) on the $i - v$ plane. The solution is the coordinate of the intersection of the two lines.

- The line specified by Eq. (5.15) is also known as the load line.

 


Figure 5.12: Graphical analysis for the circuit given in Figure 5.11.

Piecewise Linear Model

- A simpler model easier for analysis.

$$i_D(v_D) = \begin{cases} 0 & \text{if } v_D < V_{D0} \\ (v_D - V_{D0})/\gamma_D & \text{if } v_D \geq V_{D0} \end{cases} \quad (5.16)$$

Constant Voltage Drop Model

- The simplest model for analysis.
 - Forward-conducting diode exhibits a voltage drop V_D of $0.7V$.
 - The model frequently employed in the initial phase of analysis and design.

 


Figure 5.13: The piecewise linear model of the diode forward i-v characteristic.

 


Figure 5.14: The constant voltage drop model of the diode forward i-v characteristic.

5.3.2 Small Signal Model

- Small signal model is used for the applications in which a diode is biased to operate in the forward region and a small ac signal is superimposed on the dc quantities.
- Small signal analysis
 - Determine the dc bias point (or quiescent point) using the large signal models.
 - * The constant voltage drop model is commonly used.
 - Determine the small signal operation around the dc bias point by modeling the diode with a resistance.
 - * The resistance is the slope of the tangent to the exponential $i - v$ curve.

Example 5.2 Consider the circuit in Figure 5.15, where the dc voltage V_D is applied to the diode and a time varying signal $v_d(t)$ is further superimposed to the dc voltage V_D , and the corresponding graphical representation, find out the $i_D(t)$ and $v_D(t)$ of the diode.

1. The dc operation point of the diode can be found as follows:

$$I_D = I_s e^{V_D/nV_T} \quad (5.17)$$

 


Figure 5.15: Circuit for the development of the diode small signal model and the corresponding graphical representation.

2. When the small signal $v_d(t)$ is applied, the instantaneous diode current $i_D(t)$ will be

$$\begin{aligned} i_D(t) &= I_s e^{(V_D + v_d(t))/nV_T} \\ &= I_s e^{V_D/nV_T} \times e^{v_d(t)/nV_T} \\ &= I_D \times e^{v_d(t)/nV_T} \end{aligned} \quad (5.18)$$

3. If the amplitude of the signal $v_d(t)$ is kept sufficiently small, the exponential term in Eq. (5.18) can be expanded in a series.³ The small signal approximation is obtained by truncating the series after the first two terms.

$$i_D(t) = I_D \times e^{v_d(t)/nV_T} \simeq I_D \times \left(1 + \frac{v_d(t)}{nV_T} \right) \quad (5.19)$$

- Valid for signals whose amplitudes are sufficiently small, e.g., $10mV$ for the case $n = 2$ and $5mV$ for $n = 1$.⁴
- The ac current in Eq. (5.19), defined as follows, is proportional to the signal $v_d(t)$.

$$i_d(t) \equiv I_D \times \frac{v_d(t)}{nV_T} \quad (5.20)$$

- The diode small-signal resistance (or incremental resistance)⁵, $v_d(t)/i_d(t) =$

³The fourier expansion of $e^x =$.

⁴The magnitude is approximately $(1/5) \times nV_T$.

⁵Only the ac component is considered.

nV_T/I_D , is inverse proportional to the bias current I_D .

Conclusion 5.3 For diode, the small signal analysis can be performed separately from the dc analysis.

- After the dc analysis is performed, the small signal equivalent circuit is obtained by eliminating all dc sources (i.e., short-circuiting dc voltage sources and open-circuiting ac current sources.) and replacing the diode with its small-signal resistance.

Example 5.4 Consider the circuit shown in Figure 5.16 (a) for the case in which $R = 10K\ \Omega$. The power supplier V^+ has a dc value of $10V$ on which it is superimposed a $60Hz$ sinusoid of $1-V$ peak amplitude. Calculate the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it. Assume the diode to have a $0.7-V$ drop at $1-mA$ current and $n=2$.

 


Figure 5.16: Example of separating small signal analysis from dc analysis.

1. Consider dc signal only as in Figure 5.16 (b), the dc current of the diode is

$$I_D = \frac{10 - 0.7}{10} = 0.93mA$$

2. Since the dc current is very close to $1mA$, the diode voltage will be very close to the assumed $0.7V$. At this quiescent point, the diode incremental resistance γ_d is

$$\gamma_d = \frac{nV_T}{I_D} = \frac{2 \times 25}{0.93} = 53.8\ \Omega$$

3. Now we remove the dc source and replace the diode with incremental resistance as in Figure 5.16 (c). Then, the peak amplitude of v_d can be calculated as follows.


$$v_d(\text{peak}) = v_s \times \frac{\gamma_d}{R + \gamma_d} = 5.35mV.$$

4. As compared with $nV_T = 50mV$, the peak amplitude of v_d is quite small. The use of the small-signal model is justified.

5.3.3 Circuit Analysis with Diodes

Analysis of a circuit including diodes normally goes through the following procedure.

- Make plausible assumptions.
- Apply linear circuit analysis.
- Check solution and repeat the process if necessary.

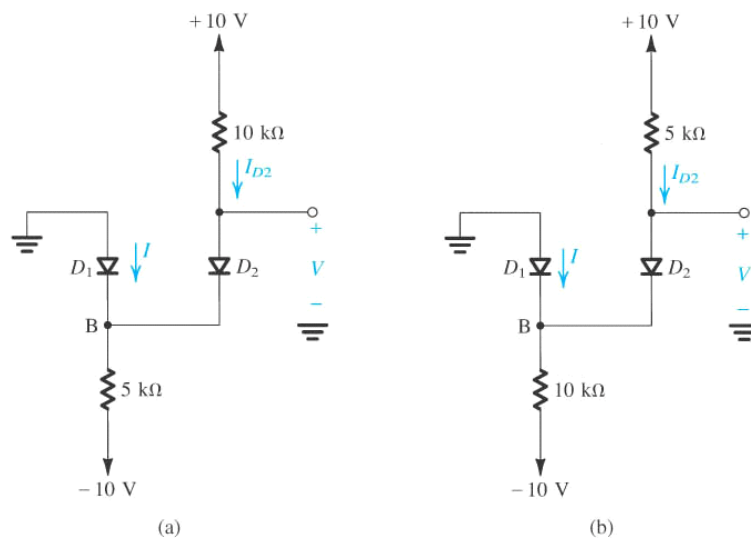

Example 5.5 Resolve the current I and the voltage V for the two circuits in Figure ??.

Case A

1. Diodes D_1 and D_2 are assumed to be forward biased and replaced with short circuits. It follows that $V_B = 0$ and $V = 0$. Consequently,

$$I_{D2} = \frac{10 - 0}{10} = 1\text{mA}.$$

2. Further, writing a node equation at the node B.

$$I + 1 = \frac{0 - (-10)}{5} \Rightarrow I = 1\text{mA}.$$

3. Thus, both D_1 and D_2 are conducting as originally assumed.

Case B

1. Diodes D_1 and D_2 are assumed to be forward biased and replaced with short circuits. It follows that $V_B = 0$ and $V = 0$. Consequently,

$$I_{D2} = \frac{10 - 0}{5} = 2\text{mA}.$$

2. Further, writing a node equation at the node B.

$$I + 2 = \frac{0 - (-10)}{10} \Rightarrow I = -1\text{mA}.$$

- 3 Since this is not possible, the assumption is invalid. To obtain a consistent solution, the assumption is modified in such a way that D_1 is off. As a result,

$$I_{D2} = \frac{10 - (-10)}{15} = 1.33\text{mA}.$$

$$V = V_B = -10 + 1.33 \times 10 = 3.3\text{V}.$$

5.4 Special Diodes

5.4.1 Zener diode

 


Figure 5.17: Symbol of Zener diode and its i - v characteristics.

- Zener diodes are specifically designed to operate in breakdown region.
 - The steep $i - v$ characteristic is ideal for voltage regulators⁶.

⁶Voltage regulators need to provide constant dc output voltages in the face of changes in load current and system power-supply voltage.

 


Figure 5.18: Model for the Zener diode.

- Parameters of Zener diodes.
 - The voltage V_Z across the diode at a testing current I_{ZT} . (The operating point)
 - The incremental resistance γ_z at the operation point.
 - The knee current I_{ZK} .
 - * The $i - v$ curve for currents greater than I_{ZK} is almost a straight line.
- Model of Zener diodes in breakdown region is specified in Eq. (5.21).
 - Applied for $I_Z > I_{ZK}$ and $V_Z > V_{Z0}$.
 - V_{Z0} is the intersection of the straight line of slope $1/\gamma_z$ and the voltage axis.

$$V_Z = V_{Z0} + \gamma_z I_Z \quad (5.21)$$

5.4.2 Switching Controlled Rectifier (SCR)

5.4.3 LED/Varactors

5.5 Applications

5.5.1 Regulator

Example 5.6 Use of the Zener diode as a Shunt Regulator which appears in parallel with the load. The 6.8-V Zener diode in Figure 5.19 is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$, $\gamma_Z = 20\Omega$, and $I_{ZK} = 0.2mA$. The supply voltage V^+ is normally 10V but can vary by $\pm 1V$.

1. From Eq. (5.21) and the given conditions, V_{Z0} can be derived as 6.7V.
2. The V_o with no loading.

$$\begin{aligned} I_Z &= I = \frac{10 - 6.7}{0.5 + 0.2} = 6.35mA \\ V_o &= V_{Z0} + \gamma_Z \times I_Z = 6.83V \end{aligned}$$

 


Figure 5.19: Use of Zener diode as a Shunt Regulator.

3. The line regulation ($\Delta V_o / \Delta V^+$) due to the $\pm 1V$ change of power supply.

$$\Delta V_o = \Delta V^+ \times \frac{\gamma_Z}{R + \gamma_Z}$$

$$\frac{\Delta V_o}{\Delta V^+} = \frac{\gamma_Z}{R + \gamma_Z} = \frac{20}{500 + 20} = 38.5 \text{ mV/V}$$

4. The load regulation ($\Delta V_o / \Delta I_L$) as a load resistor draws a current $I_L = 1 \text{ mA}$.

- Assume the total current I does not change significantly when the load is connected.

$$\Delta V_o = \gamma_Z \times \Delta I_Z = 20 \times -1 = -20 \text{ mV}$$

$$\frac{\Delta V_o}{\Delta I_Z} = -20 \text{ mV/mA}$$

5. The change of V_o when a load resistor $R_L = 2 \text{ K}\Omega$ is connected.

- Assume the total current I does not change significantly when the load is connected.
- The approximation of the load current is as follows and the change of V_o can be obtained accordingly.

$$\Delta I_Z = \frac{6.8}{2} = 3.4 \text{ mA}$$

$$\Delta V_o = \gamma_Z \times \Delta I_Z = 20 \times -3.4 = -68 \text{ mV}$$

- The accurate number from circuit analysis is $\Delta V_o = -70 \text{ mV}$.

6. The change of V_o when a load resistor $R_L = 0.5 \text{ K}\Omega$ is connected.

- It is impossible that the load would draw a current of $6.8/0.5 = 13.6 \text{ mA}$. Thus,

the diode must be cut-off. Accordingly, the V_o can be obtained as follows:

$$V_o = V^+ \times \frac{R}{R + R_L} = 5V.$$

7. The minimum value of R_L for which the diode still operates in the breakdown region.
 - The minimum voltage supply is around $9V$. At this point, the lowest current supplied is $(9 - 6.7)/0.5 = 4.6mA$ and thus the load current is $4.6 - 0.2 = 4.4mA$. The corresponding value of $R_L = 6.7/4.4 = 1.5K \Omega$.

5.5.2 Rectifier

- A diode rectifier is an essential building block of the dc power supply.
- Figure 5.20 depicts the block diagram of the dc power supply.
 - Power transformer
 - * To step the line voltage down to the required value.
 - * To minimize the risk of electric shock by providing electrical isolation between the equipment and the power line.
 - Diode rectifier
 - * Convert input sinusoid to a unipolar output.
 - * Two parameters must be specified in selecting the diodes.
 - The largest current the diode is expected to conduct.
 - The largest reverse current that is expected to withstand without breakdown. (Peak inverse voltage)
 - Filter
 - * Convert pulsating waveform to a constant output.
 - Voltage regulator
 - * To reduce the ripple
 - * To stabilize the dc output as the load current changes.

 


Figure 5.20: Block diagram of a dc power supply.

Half-Wave Rectifier

- Utilize alternate half-cycles of the input sinusoid.
- Figure 5.21 shows an example of half-wave rectifier.
 - $\text{PIV} = V_S$.
 - It may not function properly when the input signal is small.

$$v_o = \begin{cases} 0 & \text{if } V_S < V_{D0} \\ \frac{R}{R+r_D} \times (V_S - V_{D0}) & \text{if } V_S \geq V_{D0} \end{cases} \quad (5.22)$$

 


Figure 5.21: Circuit of half-wave rectifier.

Full-Wave Rectifier

- Utilize both halves of the input sinusoid.
- Figure 5.22 shows an example of full-wave rectifier.
 - When the input voltage is positive, both of the signals v_S will be positive.
 - * D_1 will conduct and D_2 will be reverse biased.
 - When the input voltage is negative, both of the signals v_S will be negative.
 - * D_1 will be reverse biased and D_2 will conduct.
 - v_o is unipolar since the current always flows through R in the same direction.
 - $\text{PIV} = 2V_S - V_D$.
 - A center-tapped transform is required.
- Figure 5.23 shows another implementation of full-wave rectifier.
 - When the input voltage is positive, the signals v_S will be positive.
 - * D_1 and D_2 will conduct; D_3 and D_4 will be reverse biased.
 - When the input voltage is negative, the signals v_S will be negative.

 


Figure 5.22: Circuit of full-wave rectifier using center-tapped transformer.

- * D_3 and D_4 will conduct; D_1 and D_2 will be reverse biased.
- v_o is unipolar since the current always flows through R in the same direction.
- $\text{PIV} = v_o + v_{D2}(\text{forward}) = V_S - 2V_D + V_D = V_S - V_D$.
- Advantages
 - * PIV is about half the value for the center-tapped implementation.
 - * A center-tapped transform is not required.
 - * Less turns are required for the secondary winding of the transformer.

 


Figure 5.23: Circuit of the bridge rectifier.

The Peak Rectifier

- The peak rectifier reduces the variation of output voltage by introducing a capacitor.
- Figure 5.24 shows the circuit of the peak rectifier.
 - The capacitor charges to the peak of the input V_P .
 - The diode cuts off and the capacitor discharges through the load R .

 


Figure 5.24: Circuit of the peak rectifier.

- * The output $v_o(t)$ during the discharge.⁷

$$v_o(t) = V_P e^{-t/RC} \quad (5.23)$$

- * The voltage drop V_γ due to the discharge.⁸

$$\begin{aligned} V_P - V_\gamma &\simeq V_P e^{-T/RC} \\ \Rightarrow V_\gamma &= V_P (1 - e^{-T/RC}) \simeq V_P \frac{T}{RC} \end{aligned} \quad (5.24)$$

- To keep V_γ small, we must select a capacitor C so that $RC \gg T$.

- * The alternative expression of V_γ .

$$V_\gamma \simeq V_P \frac{T}{RC} = \frac{I_L}{fC} \quad (5.25)$$

- $I_L = V_P/R$ is the load current when V_γ is small.
- $f = 1/T$ is the frequency of the voltage supplier.
- To keep V_γ small, we can either select a large capacitor C or increase the frequency of the voltage supplier.

- The discharge continues until v_I exceeds the capacitor voltage.

⁷The node equation when the diode is cut off: $C \frac{dv_o(t)}{dt} + \frac{v_o(t)}{R} = 0$.

⁸ $e^x =$

5.5.3 Limiting

- Limiter (also known as clipper) limits the voltage between the two output terminals.

 


Figure 5.25: Transfer characteristic for a limiter circuit.

- Eq. (5.26) and Figure 5.25 show the transfer function of limiter.

$$v_o = \begin{cases} L_- & \text{if } v_I < L_-/K \\ K v_I & \text{if } L_-/K \leq v_I \leq L_+/K \\ L_+ & \text{if } v_I > L_+/K \end{cases} \quad (5.26)$$

- Diode can be combined with resistors to implement limiters.
 - Figure 5.26 (a) and (b) are single limiters.
 - * Single limiter works for either positive or negative peak.
 - Figure 5.26 (c) is a double limiter.
 - * Double limiter works for both positive and negative peaks.
 - Figure 5.26 (d) shows that the threshold and saturation current can be controlled by using strings of diodes and/or by connecting a dc voltage in series with the diode.
 - Figure 5.26 (e) shows another double limiter using double-anode Zener.

5.5.4 Clamping

- Diodes can be used for the circuit of dc restorer (also known as clamped capacitor).
- Figure 5.27 shows an example of dc restorer with no load.
 - When $v_I = -6V$, the capacitor will charge to a voltage v_C .
 - * v_C is equal to the magnitude of the most negative peak, i.e., $6V$.
 - * The polarity of v_C is indicated as in Figure 5.27.

 


Figure 5.26: A variety of basic limiting circuits.

- * The diode is turned off and the capacitor retains its voltage indefinitely.
- When $v_I = 4V$, the output $v_C = v_I + v_C = 10V$.
- Figure 5.28 shows the example of dc restorer with a load resistor R .
 - As $t_0 < t < t_1$, the output voltage falls exponentially with time constant RC .
 - At t_1 , the input decreases by V_a and the output attempts to follow.
 - * The diode conduct heavily and quickly discharge the capacitor.
 - At the end of the period t_1 to t_2 , the output voltage is around $-0.5V$.

 


Figure 5.27: The clamped capacitor or dc restorer with a square-wave input and no load.

 


Figure 5.28: The dc restorer with a load resistor R .

5.5.5 Digital Logic

- Diodes can also be used for logic gates as shown in Figure 5.29.

 


Figure 5.29: Digital logic gates: (a) OR gate; (b) AND gate. (Positive logic system)